

GATE 2022 IN 36

EE23BTECH11065 - prem sagar

Question:

A signal $V_{in}(t)$ shown is applied from $t=0\text{ms}$ to $t=6\text{ms}$ to the circuit shown. Given the initial voltage across capacitor is 0.3V , and that the diode is ideal, the open circuit voltage $V_{out}(t)$ at $t=5\text{ms}$ is

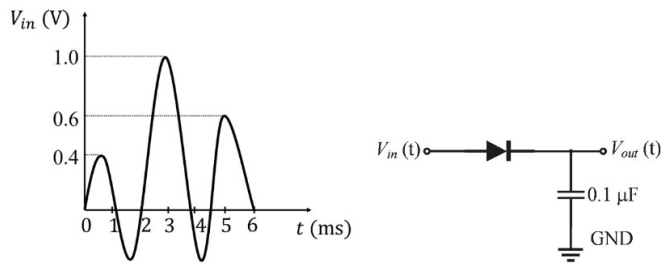


Fig. 1.

Solution:

Symbol	Value	Description
$V_{in}(t)$		input signal
$V_c(t)$		voltage across capacitor
$V_c(0)$	0.3V	initial voltage across capacitor
$v_{out}(t)$		open circuit voltage

TABLE I
INPUT PARAMETERS

From Table 1
the circuit is a positive peak detector circuit

$$V_c(t) = V_{in}(t) - V_{out}(t) \quad (1)$$

as diode is ideal
during positive half cycle of input signal it conducts
allowing capacitor to charge to the peak voltage of
input

$$V_{out}(t) = V_c(t) \quad (2)$$

$$= 1\text{V} \quad (3)$$

once the capacitor is charged to 1V it retains this
voltage due to ideal diode's behaviour and open
circuit condition. \therefore at $t=5\text{ms}$

$$V_{out} = 1\text{V} \quad (4)$$